

Total number of printed pages-4

**3 (Sem-5/CBCS) PHY HE4**

**2021**

**(Held in 2022)**

**PHYSICS**

**(Honours Elective)**

Paper : PHY-HE-5046

**(Physics of Device and Instruments)**

Full Marks : 60

Time : Three hours

**The figures in the margin indicate  
full marks for the questions.**

1. Answer the following questions :  $1 \times 7 = 7$

(a) Write the full form of MOSFET.

(b) Capacitor is a

(i) high-pass filter

(ii) low-pass filter

(iii) both high and low-pass filters

Contd.

- (c) What does the USB stand for?
- (d) What is the difference between an astable multivibrator and a monostable multivibrator?
  - (i) The astable is free running
  - (ii) The astable needs to be clocked
  - (iii) The monostable is free running
- (e) What happens when the modulation index is greater than 1?
- (f) Mention *two* advantages of CMOS technology.
- (g) At critical frequency at which the response drop from the pass band is
  - (i)  $-20\text{ dB}$
  - (ii)  $-3\text{ dB}$
  - (iii)  $20\text{ dB}$

2. Answer the following questions briefly :  
 $2 \times 4 = 8$

- (a) Give *two* differences between MOSFET and JFET.
- (b) Explain active and passive filter. Give an example of each.
- (c) What is RS232 communication?

- (d) Calculate the carrier frequency of an AM wave when its highest frequency component is  $850\text{ Hz}$  and the bandwidth of the signal is  $50\text{ Hz}$ .

3. Answer **any three** of the following questions :  
 $5 \times 3 = 15$

- (a) Give the circuit diagram and explain the working of a dc power supply using bridge rectifier and L-section filter.
- (b) Explain the I-V characteristic of UJT. Explain its use as a relaxation oscillator.
- (c) Give a short note on short circuit protection.
- (d) What do you mean by USB standard? Give details of the USB 2.0.
- (e) What is a tunnel diode? Explain its V-I characteristics.

4. Answer **any three** of the following questions :

- (a) What is a sequential logic circuit? Draw the circuit diagram of a monostable multivibrator and explain its operation.  
 $2 + (2 \times 6) = 10$

- (b) Define low-pass filter and high-pass filter. Write the differences between them.  $5+5=10$
- (c) With a neat sketch, describe the construction of an  $n$ -channel JFET. Explain the principle of operation.  $5+5=10$

**Or**

Explain with neat sketch the structure and working of  $p$ -channel enhancement type MOSFET.  $10$

- (d) What is an IC circuit? What are the basic steps of IC fabrication? Explain etching and masking in case of IC fabrication.  $5+5=10$
- (e) Discuss the working of an exclusive-OR phase detector. Give the schematic diagram of PLL and explain its working.  $5+5=10$
- (f) What is amplitude modulation? Show that the amplitude modulation wave consists of a carrier and two sidebands.  $3+7=10$

**Or**

Draw the circuit of a CE amplitude modulation and derive the expression for its output.  $10$