

Total number of printed pages-4

3 (Sem-5/CBCS) PHY HE 4

2025

**PHYSICS**

(Honours Elective)

Paper : PHY-HE-5046

**(Physics of Devices and Instruments)**

Full Marks : 60

Time : Three hours

**The figures in the margin indicate full marks for the questions.**

1. Answer the following questions :  $1 \times 7 = 7$

(a) At critical frequency at which the response drop from the pass band is

(i)  $-20 \text{ dB}$

(ii)  $-3 \text{ dB}$

(iii)  $20 \text{ dB}$

(b) Mention *two* advantages of CMOS technology.

- (c) What happens when the modulation index is greater than 1 ?
- (d) What is the difference between an astable multivibrator and a monostable multivibrator ?
- (i) The astable is free running
- (ii) The astable needs to be clocked
- (iii) The monostable is free running
- (e) What does the USB stand for ?
- (f) Capacitor is a
- (i) high-pass filter
- (ii) low-pass filter
- (iii) both high and low-pass filters
- (g) Write the full form of MOSFET.

2. Answer the following questions briefly :  
2×4=8

- (a) Calculate the carrier frequency of an AM wave when its highest frequency component is 850 Hz and the bandwidth of the signal is 50 Hz.
- (b) What is RS232 communication ?
- (c) Explain active and passive filter. Give an example of each.

- (d) Give *two* differences between MOSFET and JFET.

3. Answer **any three** of the following questions :  
5×3=15

- (a) What is a tunnel diode? Explain its V-I characteristics.
- (b) What do you mean by USB standard? Give details of the USB 2.0.
- (c) Give a short note on short-circuit protection.
- (d) Explain the I-V characteristic of UJT. Explain its use as a relaxation oscillator.
- (e) Give the circuit diagram and explain the working of a dc power supply using bridge rectifier and L-section filter.

4. Answer **any three** of the following questions :

- (a) What is amplitude modulation? Show that the amplitude modulation wave consists of a carrier and two sidebands.  
3+7=10

**Or**

Draw the circuit of a CE amplitude modulation and derive the expression for its output.  
10

- (b) Discuss the working of an exclusive-OR phase detector. Give the schematic diagram of PLL and explain its working.  $5+5=10$
- (c) What is an IC circuit? What are the basic steps of IC fabrication? Explain etching and masking in case of IC fabrication.  $5+5=10$
- (d) With a neat sketch, describe the construction of an  $n$ -channel JFET. Explain the principle of operation.  $5+5=10$

**Or**

Explain with neat sketch the structure and working of  $p$ -channel enhancement type MOSFET.  $10$

- (e) Define low-pass filter and high-pass filter. Write the differences between them.  $5+5=10$
- (f) What is a sequential logic circuit? Draw the circuit diagram of a monostable multivibrator and explain its operation.  $2+(2+6)=10$
-